

433MHz RF Transmission and Reception system

Designed by RM

This project file details a microcontroller based data transmission system utilizing rudimentary 433MHz transmission modules. The system consists of a transmitter and receiver, both using ATTiny13 8-pin microcontrollers. The method used for transmission is a Pulse-width based method, and the 4-bit data words that are transmitted are generated using switches and displayed on LEDs.


It should be noted that this system could be adapted, with minor additions or modifications, to perform more useful tasks such as turning on remote equipment.

Contents


1. Transmitter Schematic, PCB and Layout
2. Receiver Schematic, PCB and Layout
3. Assembly code
4. How it works
5. Misc and Photo of completed devices

Transmitter

Basic Digital Transmitter

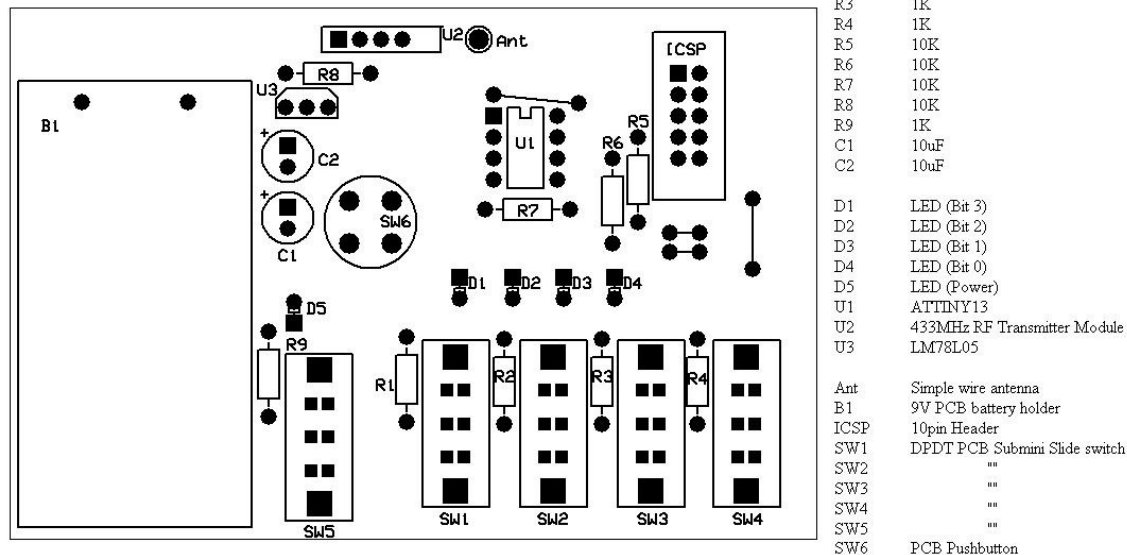


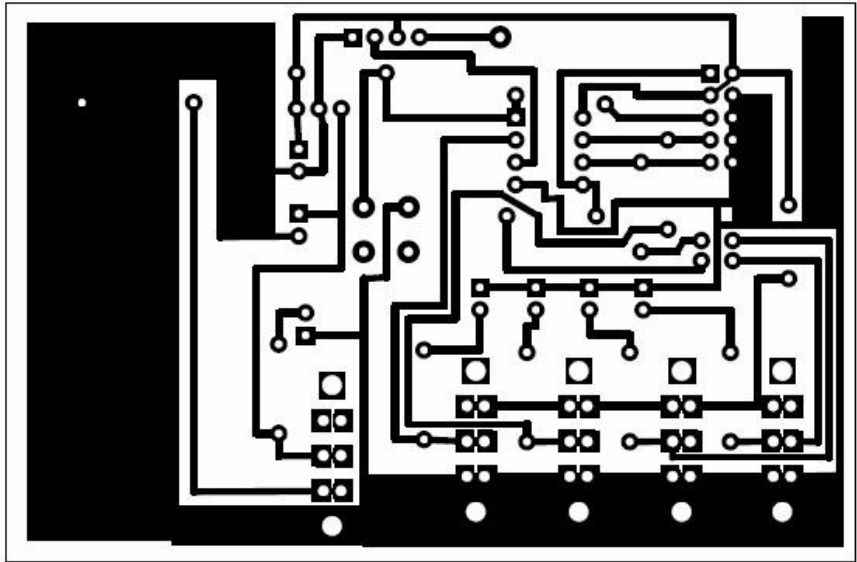The specified 433MHz antenna length is 17.2cm.




Note: PCB not to scale. When scaling for printing, width from border to border should measure 3.8 Inches, and height from border to border should measure 2.5 Inches.

Receiver

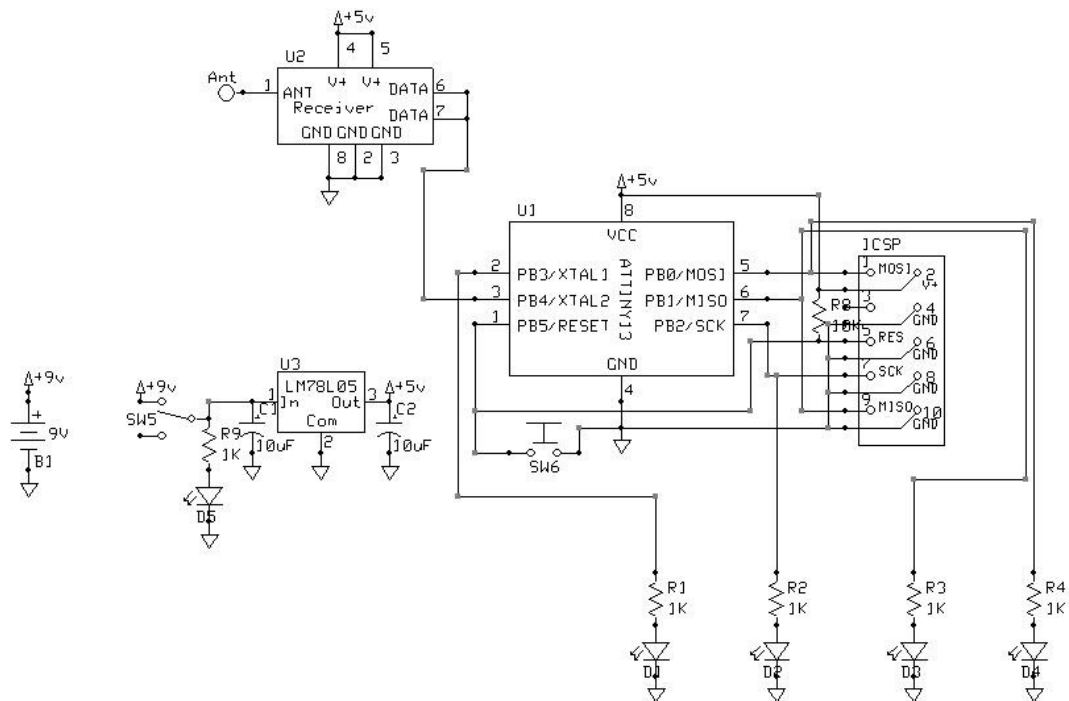


Transmitter

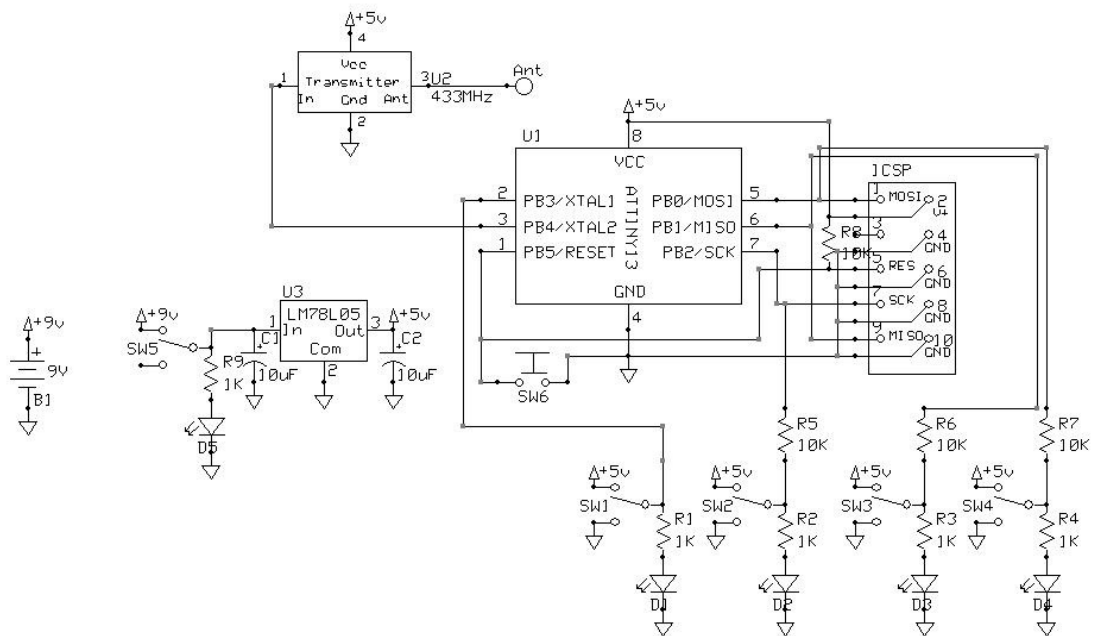

Receiver

Basic Digital Receiver

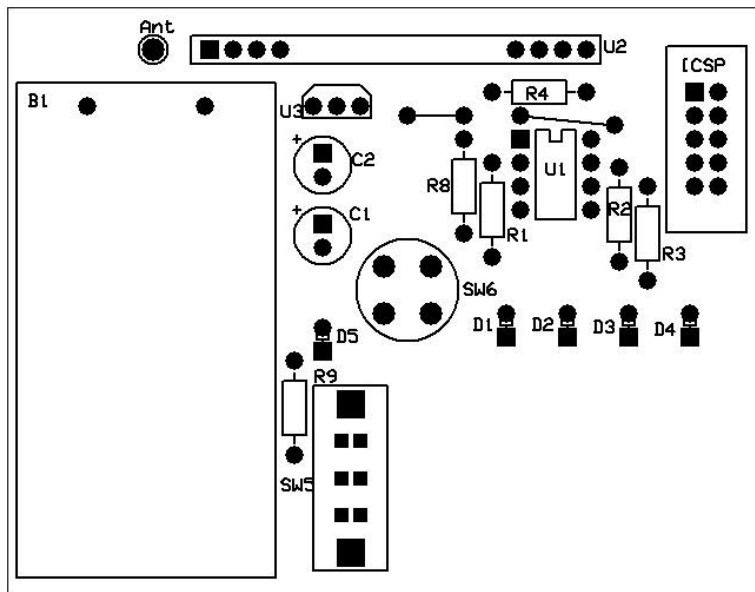


Parts:

R1 1K
R2 1K
R3 1K
R4 1K
R8 10K
R9 1K
C1 10uF
C2 10uF

D1 LED (Bit 3)
D2 LED (Bit 2)
D3 LED (Bit 1)
D4 LED (Bit 0)
D5 LED (Power)

U1 ATTINY13
U2 433MHz RF Receiver module
U3 LM78L05

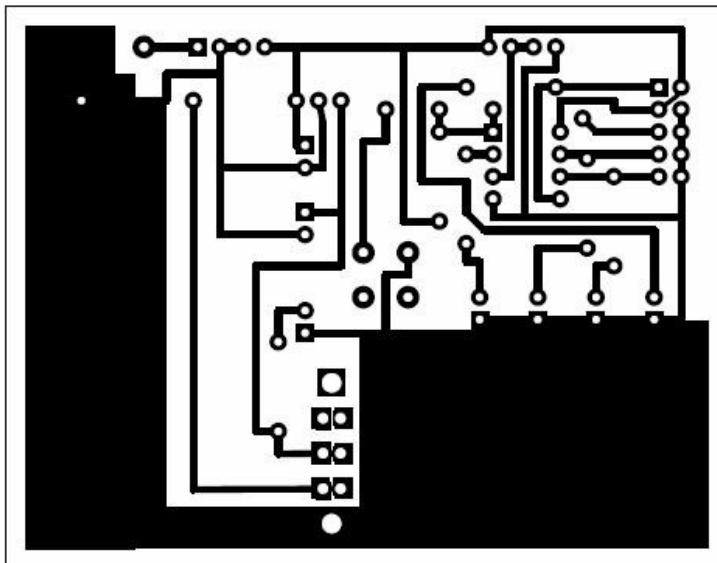Ant Simple wire antenna
B1 9V
ICSP 10pin Header
SW5 DPDT PCB Submini Slide switch (Power)
SW6 PCB Pushbutton (Reset)



Note: PCB not to scale. When scaling for printing, width from border to border should measure 3.2 Inches, and height from border to border should measure 2.5 Inches.

Assembly Code

The programs for the receiver and transmitter were written using assembly language, and programmed into the microcontrollers using AVR Studio 4.12 and PongProg2000 (with ATtiny13 support). The programming hardware was a DIY parallel port programming dongle.

Transmitter Code:

```
.include "tn13def.inc"
.def temp = r16
.def temp2 = r17
.def count = r18
.def temp3 = r19
.def temp4 = r20

reset:
ldi    temp, 0b00010000
out     DDRB, temp
ldi     temp, low(RAMEND)
out     SPL, temp
ldi     temp, 0b00000101
out     TCCR0B, temp

main:
in      temp, PINB
ldi     count, 5

sbi     PORTB, 4 ;start pulse
rcall   delay
rcall   delay
rcall   delay
cbi     PORTB, 4
rcall   delay
rcall   delay
rcall   delay

sendloop:
dec     count
breq    endtrans
sbrs    temp, 3
rjmp    send0
send1:
sbi     PORTB, 4
rcall   delay
rcall   delay
cbi     PORTB, 4
rcall   delay
rcall   delay
lsl     temp
rjmp    sendloop
send0:
sbi     PORTB, 4
rcall   delay
cbi     PORTB, 4
rcall   delay
lsl     temp
rjmp    sendloop

endtrans:
rjmp    endtrans

delay:
ldi     temp3, 221
ldi     temp4, 16
delaya:
dec     temp3
brne    delaya
ldi     temp3, 221
dec     temp4
```

```
brne    delaya
ret
```

Receiver Code:

```
.include "tn13def.inc"
.def temp = r16
.def temp2 = r17
.def count = r18
.def data = r19

.equ startbitlength = 30
.equ bit1length = 21
.equ bit0length = 11
.equ startcutoff = 36
.equ bit1cutoff = 27
.equ bit0cutoff = 15
.equ pulsecutoff = 5

;PB0-3 - LEDs (out)
;PB4 - Data (in)

reset:
ldi     temp, 0b00001111
out     DDRB, temp
ldi     temp, RAMEND
out     spl, temp
ldi     temp, 0b00000101
out     TCCR0B, temp

main:
out     PORTB, data ;output data

sbis    PINB, 4    ;wait for start bit
rjmp    main

ldi     temp, 0
out     TCNT0, temp
parta:
sbic    PINB, 4
rjmp    parta

in      temp, TCNT0
cpi     temp, startcutoff ;test pulse size
brlo    partb
rjmp    main
partb:
cpi     temp, bit1cutoff
brge    partc
rjmp    main

partc:
;decoding subroutine
ldi     count, 4
clr     data

partd:
sbis    PINB, 4    ;wait for bit
rjmp    partd

ldi     temp, 0
out     TCNT0, temp

parte:
sbic    PINB, 4
rjmp    parte

in      temp, TCNT0
cpi     temp, bit1cutoff
brlo    partf
rjmp    main

partf:
```

```

    cpi    temp, bit0cutoff
    brlo   partg
    lsl    data
    sbr    data, 1 ;put a 1 in data register
    dec    count
    breq    main    ;all data received
    rjmp   partd    ;or continue decoding
```

```

partg:
    lsl    data
    cbr    data, 1
    dec    count
    breq    main    ;all data received
    rjmp   partd    ;or continue decoding
```

How it works

Instructions

To operate the devices, you enter a 4-bit word using the switches on the transmitter, and then press the reset button. Providing you are within range, the 4-bit word will appear on the LEDs on the receiver.

The system works using a Pulse-width based method, which uses different sized pulses to indicate 'start' '1' and '0'. The start bit indicates a new transmission word is arriving. The program cycles through each bit of the word, and creates the appropriate sized pulse for each one. The receiver times the lengths of each pulse, and then places the appropriate bit in the data register. The reason this method was used, was because the rudimentary RF modules used require the amount of 'on' and 'off' time to be near the same to function correctly.

Miscellaneous

Programming

If you do not have a commercial AVR programmer, you can build your own very simple one, using the details from the following website: <http://www.tothemax.web1000.com> – under “PIC and AVR”. You will need to download PonyProg2000 and get the ATTiny13 support executable.

Parts

The 433MHz RF Modules are available from Jaycar Electronics (<http://www.jaycar.com.au>), and cost \$AUS20 a pair.

Hex Files

Compiled Hex files for use with PonyProg are available at these addresses:

http://www.geocities.com/race_driver205/trans.hex

http://www.geocities.com/race_driver205/receiv.hex

Use of this document

If you want to use the information in this document in commercial designs, go for your life. If you make millions and retire in a beach-front villa with a super-model wife and a Ferrari, I’m cool with that.

Modifications

The most obvious modification is to change the “rjmp endtrans” instruction in the transmitter program to “rjmp main”. This will mean you don’t have to press the pushbutton to send each data word, and flicking the switches will change the receiver outputs instantly.

Other Uses

The transmission method could easily be modified to allow for transmission of 8-bit or greater words. The key things to change would be the ‘count’ register initial value, and the bit position that is read from.

Help

If you have any questions, please forward them to tothemax6@hotmail.com. I guarantee that I built these devices myself and that they work correctly, so debugging questions are regrettably unlikely to be answered.



The Finished Gear